



# ***North South University***

## ***Department of Electrical & Computer Engineering***

### **Lab Report**

<b>Experiment No:</b>	2
<b>Experiment Title:</b>	Design a 4-bit by 4-bit Binary Multiplication Unit
<b>Course Code:</b>	CSE332L
<b>Course Name:</b>	Computer Organization & Architecture Lab
<b>Name &amp; ID:</b>	Nawal Ayesha Khan, 1911301042
<b>Date of Experiment:</b>	10.3.2021
<b>Date of Submission:</b>	10.3.2021

★ Objectives:

- Understanding behaviour of computational multiplier designed as part of the experiment.
- Understanding the theory and implementing multiplication unit.
- Check multiplying bits and show sum outputs.

★ Equipment:

- 4 x 7408 AND IC
- 3 x 7483 4-bit Adder IC
- Trainer board
- Wires

★ Block diagram:

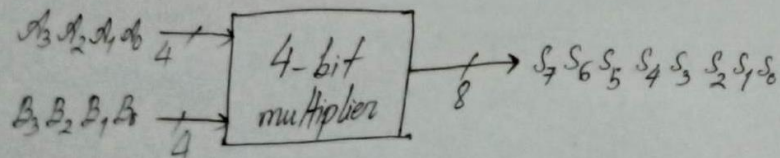


Fig 1: Block diagram for 4x4 bit multiplier circuit.


★ Truth table:

Multiplicand				Multiplier				Product								Results <del>in</del> decimal
B4	B3	B2	B1	A4	A3	A2	A1	S8	S7	S6	S5	S4	S3	S2	S1	in decimal
1	0	0	0	1	0	0	1	0	1	0	0	1	0	0	0	$8 \times 9 = 72$
0	1	0	1	0	0	1	0	0	0	0	0	1	0	1	0	$5 \times 2 = 10$
0	1	1	1	0	0	1	1	0	0	0	1	0	1	0	1	<del><math>4 \times 3 = 21</math></del> $7 \times 3 = 21$
0	1	0	0	1	0	0	0	0	0	1	0	0	0	0	0	<del><math>4 \times 8 = 32</math></del>
0	1	0	1	0	1	1	0	0	0	0	1	1	1	1	0	$5 \times 6 = 30$
1	0	0	1	0	1	0	0	0	0	1	0	0	1	0	0	$9 \times 8 = 72$
1	1	1	1	1	0	1	1	1	0	1	0	0	1	0	1	$15 \times 11 = 165$

Table: Truth table for experimental values  
of product of multiplication

**Circuit diagram:**

**Fig 2:** Circuit diagram of 4-bit binary multiplier

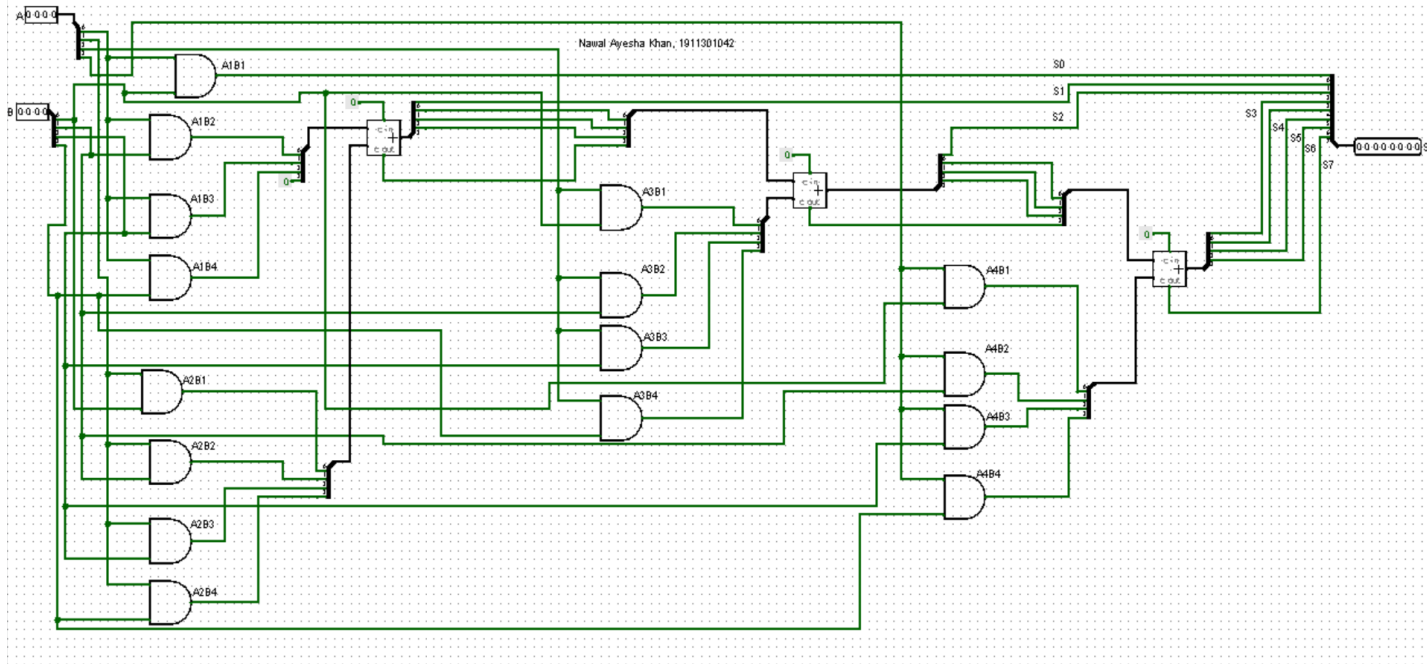

\* Discussion: In this experiment, we learned about the 4-bit multiplier using a 4-bit adders and AND gates. We tested the inputs and validated them using the truth table. AND IC is used ~~is used~~ to multiply individual bits of the inputs, and the 4-bit adders are used to add the partial products. Outputs are connected to inputs of next 4-bit adders to sum up the partial products. The ICs are placed on a trainer board, and test the experiment using input switches and output LEDs. Multiple input combinations are applied and outputs are observed and verified according to the truth table. As the outputs match the theoretical ones in the table, the multiplier works as designed, and the experiment is successful.