



North South University

Department of Electrical & Computer Engineering

Lab Report

Experiment No:	5
Experiment Title:	Design of an ALU
Course Code:	CSE332L
Course Name:	Computer Organization & Architecture Lab
Name & ID:	Nawal Ayesha Khan, 1911301042
Date of Experiment:	21/4/2021
Date of Submission:	23/4/2021

- * Objectives:
 - Designing a 16-bit ALU
 - Implementing AND, OR, ADD, SUB operations in 1-bit ALU
 - Designing a 16-bit ALU using 1-bit ALUs

* Equipment: Logisim tools

* Block diagram:

 


Figure 1. Block diagram for 16-bit ALU

* Control table:

ALUOp	Function
000	AND
001	OR
010	ADD
011	SUB

Table 1. Control selections for execution of instructions in 16-bit ALU.

Circuit diagram:

Figure 2: Circuit diagram of 1-bit ALU


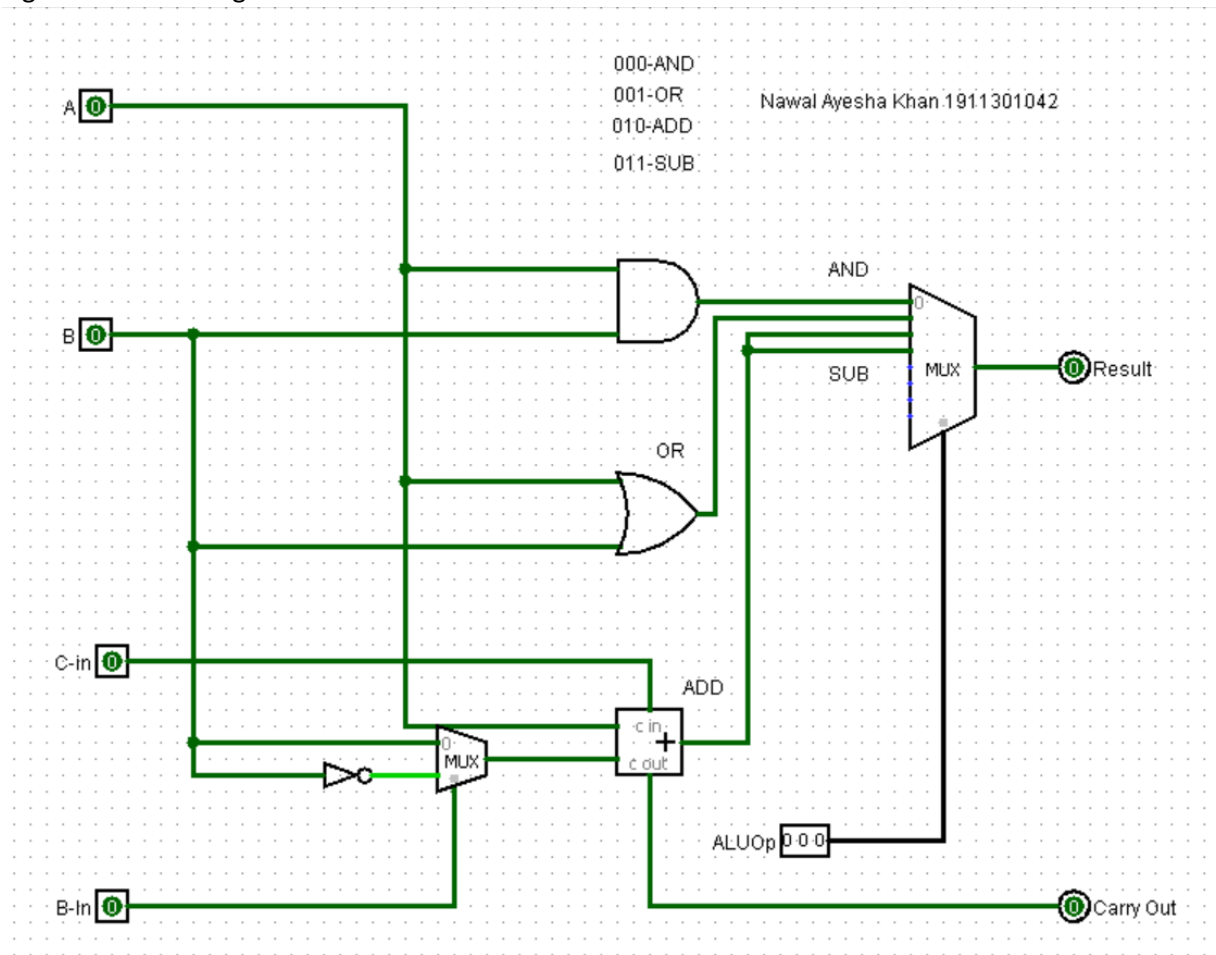


Figure 3: Circuit diagram of 16-bit ALU

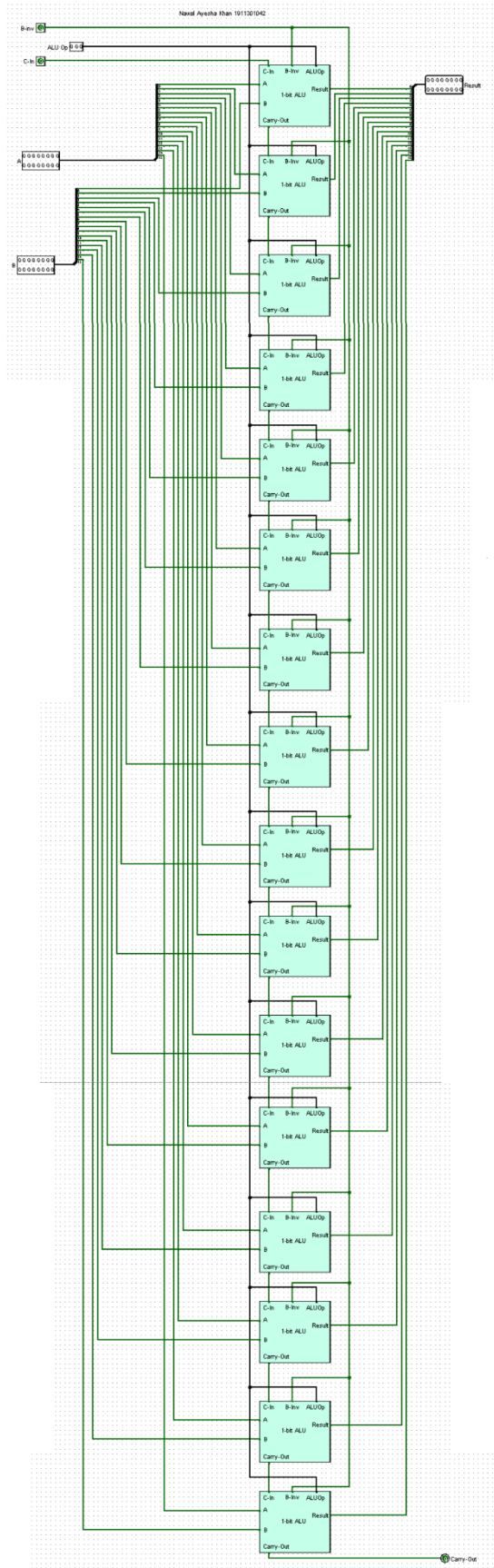

★ Discussion. In this experiment, we learned about designing a 16-bit ALU, using 16 ~~4~~ 1-bit ALUs. The experiment was simulated on Logisim using multiplexers, full-adders, and basic logic gates. Multiplexer inputs for ALUOp are chosen based on which operation has to be carried out. We ~~test~~ test the circuit using various input values and observed the corresponding outputs. There are no difference between theoretical and experimental values as it was done as a simulation. Since the outputs match theoretical ones and the 16-bit ALU works as designed, we can conclude experiment was successful.